

Combinational Logic Design

GRAB A
HANDOUT

Today's lecture


- **Combinational Logic**
 - Different Representations of Boolean Functions (review)
- **How to design any circuit**
 - Write a truth table
 - Sum-of-Products implementation
 - Example
- **Other gates you should know about (XOR, NAND, NOR)**
- **Divide-and-Conquer design**

Combinational Logic

- **Definition:** Boolean circuits where the output is a pure function of the present input only.
- Circuits made up of gates, that don't have any feedback
 - No feedback: **outputs** are not connected to **inputs**
 - If you change the inputs, *and wait for a while*, the correct outputs show up.
 - Real circuits have delays (more on this later)
- Can be represented by Boolean Algebra

Four representations of Boolean functions

- Equivalent functionality

 

- Relatively mechanical to translate between these formats

A fifth representation

■ An English description/specification

Example: A sandwich shop has the following rules for making a good (meat) sandwich:

- (1) All sandwiches must have at least one type of meat.
- (2) Don't put both roast beef and ham on the same sandwich.
- (3) Cheese only goes on sandwiches that include turkey.

Write a Boolean expression for the allowed combinations of sandwich ingredients using the following variables:

c = cheese

h = ham

t = turkey

r = roast beef

English → Truth Table example

- **Most reliable method**

1. Write a truth table
2. Every row evaluating to 1 becomes a term
3. OR all the terms together

- **This will give an un-optimized expression**


- (we can write computer programs to optimize expressions)
 - (or better yet, use the ones that other people wrote...)
- (we can't write programs to design circuits for us.)

Sum of Products (SOP) form

- A useful way to represent any Boolean expression
- A **sum of products (SOP)** expression contains:
 - only OR (sum) operations at the “outermost” level
 - Each term that is summed must be a product of literals


$$f(x,y,z) = \underline{y'} + \underline{x'yz'} + \underline{xz}$$

 - The advantage is that any sum of products expression can be implemented using a **two-level circuit**
 - literals and complements at “0th” level
 - AND gates at the first level
 - a single OR gate at the second level



Truth tables to Boolean expressions

 1. **For each row in truth table where output is 1**
 - Write a product term that is true for that set of inputs
 - And only for that set of inputs



- This product will include each terminal exactly once
2. **OR all the product terms together**
product-term1 + product-term2 + product-term3 + ...

Truth table -> Boolean -> gates example

Step 1. Write a truth table

Rules:

- one of h,t,r*
rxh
c&t
- (1) must have at least one meat.
 - (2) not both roast beef and ham.
 - (3) cheese only if turkey.

Ingredients:

- c = cheese
- h = ham
- t = turkey
- r = roast beef

c	h	t	r	f(..)					
0	0	0	0	0					
0	0	0	1	1					
0	0	1	0	1					
0	0	1	1	1					
0	1	0	0	0					
0	1	0	1	0					
0	1	1	0	1					
0	1	1	1	1					
1	0	0	0	0	a	b	c	d	e
1	0	0	1	0	0	0	1	0	1
1	0	0	1	0	1	0	1	0	1
1	0	1	0	1	1	1	0	1	1
1	0	1	1	1	1	1	0	0	1
1	1	0	0	0					
1	1	0	1	0					
1	1	1	0	1					
1	1	1	1	0					

$\overline{c'h't'r}$

Step 2. Every 1 becomes a term

Truth table -> Boolean -> gates example

①

Step 1. Write a truth table

Rules:

- (1) must have at least one meat.
- (2) not both roast beef and ham.
- (3) cheese only if turkey.

Ingredients: c = cheese
h = ham
t = turkey
r = roast beef

c	h	t	r	f(..)	
0	0	0	0	0	
0	0	0	1	1	c'h't'r
0	0	1	0	1	c'h't'r'
0	0	1	1	1	c'h't'r
0	1	0	0	1	c'ht'r'
0	1	0	1	0	
0	1	1	0	1	c'htr'
0	1	1	1	0	
1	0	0	0	0	
1	0	0	1	1	
1	0	1	0	1	ch't'r'
1	0	1	1	1	ch't'r
1	1	0	0	1	
1	1	0	1	0	
1	1	1	0	1	chtr'
1	1	1	1	0	

②

Step 2. Every 1 becomes a term

Truth table -> Boolean -> gates example

Step 3. OR all the terms together

c	h	t	r	f(..)
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

$c'h't'r$

$c'h't'r'$

$c'h'tr$

$c'ht'r'$

$c'htr'$

$ch'tr'$


$ch'tr$

$chtr'$

$c'h't'r + c'h't'r' + c'h'tr + \dots$


Truth table -> Boolean -> gates example
 
$$\underline{c'h't'r} + \underline{c'h't'r'} + c'h't'r + c'ht'r' + c'ht'r + ch't'r' + ch't'r + chtr'$$



Truth table -> Boolean -> gates example
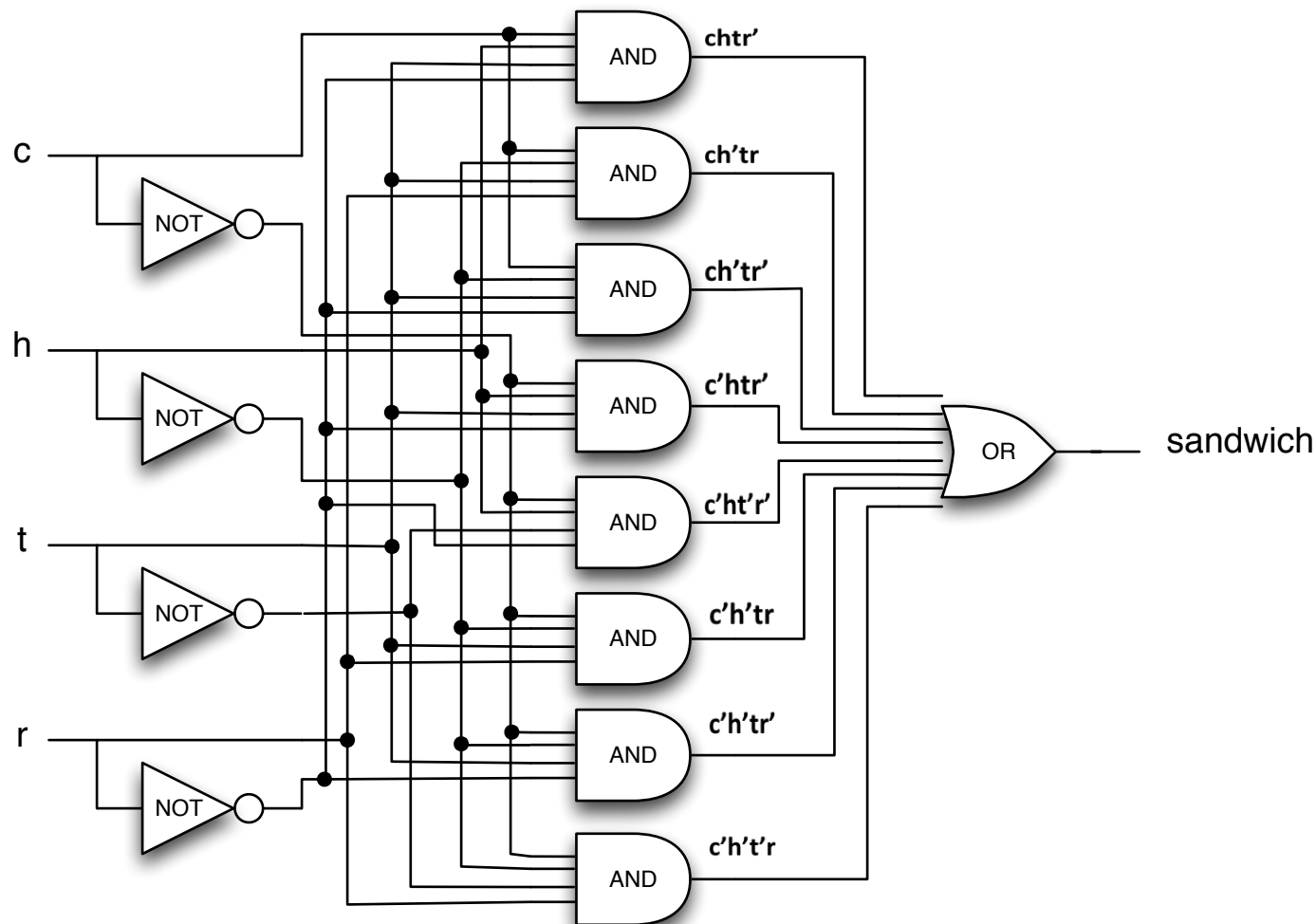
$$c'h't'r + \overset{(1+0)}{\overset{(0+1)}{c'h't(r+r)}} + c'ht'r' + c'ht'r + ch't'r' + ch't'r + chtr'$$



Three other notable 2-input functions

- Remember this table?

		AND															
x	y	f0	f1	f2	f3	f4	f5	f6	f7	f8	f9	f10	f11	f12	f13	f14	f15
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

XOR
EXCLUSIVE
OR

NOR

NAND

Additional Boolean operations

Operation:

NAND
(NOT-AND)

NOR
(NOT-OR)

XOR
(eXclusive OR)

Expressions:

$$(xy)' = x' + y'$$

$$(x + y)' = x'y'$$

$$x \oplus y = x'y + xy'$$



Truth table:

x	y	$(xy)'$
0	0	1
0	1	1
1	0	1
1	1	0

x	y	$(x+y)'$
0	0	1
0	1	0
1	0	0
1	1	0

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

Logic gates:

  

XOR gates

$$a \oplus b \oplus c \oplus d, 1 \leftarrow 1$$

$((a=1, b=0), c=1, d=1)$

- A two-input XOR gate outputs true when exactly one of its inputs is true:

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

$$\underline{x \oplus y} = x'y + xy'$$

1

- XOR corresponds more closely to typical English usage of “either ... or,” *either of the two, but not neither nor both.*
- Several fascinating properties of the XOR operation:

$x \oplus 0 = x$	$x \oplus 1 = x'$
$x \oplus x = 0$	$x \oplus x' = 1$
$x \oplus (y \oplus z) = (x \oplus y) \oplus z$	[Associative]
$x \oplus y = y \oplus x$	[Commutative]

$$x \text{ XOR } y = x' \text{ XOR } y'$$

a) False


b) True

Divide-and-Conquer Design

■ Consider the following problem

- You are building system to help avoid train collisions on subways.
- Each of the 28 segments of track:
 - Senses if there is a train on it ($T = 1$) or no train ($T = 0$)
 - Has a red/yellow/green stoplight, where exactly 1 light is on at a time
 - The red light is on ($R = 1$) if there is a train in the next segment
 - Otherwise, yellow is on ($Y = 1$) if a train is 2 segments away
 - Else, green is on ($G = 1$)

 ■ We could implement this as one big circuit.






Why would that be a bad idea?


very large truth table

Divide-and-Conquer Design

- Instead build a module:

 

- And replicate:

 

What is $Y(Xin, Yin)$?

a) $Xin \bullet Yin'$

b) $Xin' \bullet Yin$

c) $Xin + Yin'$

d) $Xin' + Yin$

e) $Xin \oplus Yin$

What is $G(X_{in}, Y_{in})$?

- a) X_{in} AND Y_{in}
- b) X_{in} OR Y_{in}
- c) X_{in} XOR Y_{in}
- d) X_{in} NAND Y_{in}
- e) X_{in} NOR Y_{in}