

Finite State Machine

pick up
a handout

Today's lecture

- **Goal: Build a sequential circuit from a state diagram**
 - Step 0: Problem specification
 - Step 1: Build the state diagram
 - Step 2: Build the state table
 - Step 3: Build the sequential circuit using D flip-flops
- **Timing diagram**
- **Another example: Sequence recognizer**

If a combinational logic circuit is an implementation of a Boolean function, then a sequential logic circuit can be considered an implementation of a finite state machine.

Step 0: Problem Specification

- We have a candy machine that dispenses candies that cost 15-cents
 - Accepts
 - nickels (5-cents)
 - dimes (10-cents)
 - Dispenses a candy if the balance is ≥ 15 -cents
 - When the customer overpays
 - the machine does not return change, but
 - keeps the balance for future transactions



Step 1: Build the State Diagram

Inputs

nickel: 5 cents
dime: 10 cents

Outputs


candy = c $\left\{ \begin{array}{l} 0 \text{ No candy} \\ 1 \text{ Candy} \end{array} \right.$

State identification

- A Got 0: Balance = 0
- B Got 5: Balance = 5
- C Got 10: Balance = 10
- D Got 15: Balance = 15
- E Got 20: Balance = 20

d n		
0 0		No coin
0 1		nickel
1 0		dime
1 1	c	not allow
0		n → candy
1		candy

Step 1: Build the State Diagram

 

Step 1: Build the State Diagram

What are the transitions for state Got-15?


A: d'n': Got0; d'n: Got5; dn': Got10

B: d'n': Got15; d'n: Got5; dn': Got10


C: d'n': Got0; d'n: Got0; dn': Got0

D: d'n': Got0; d'n: Got20; dn': Got20

Inputs: d'n', d'n, dn'

 


Step 1: Build the State Diagram

 


Inputs: $d'n'$, $d'n$, dn'

Step 1: Build the State Diagram

 

Output: c or c'

Step 2: Build a State Table

 

First 3 entries of the table:

A: A,D,E


B: B,C,D

C: A, B,C

D: A,B,E


Current State	Input	Next State
A	d'n'	A
A	d'n	B
A	dn'	C
B	d'n'	
B	d'n	
B	dn'	
C	d'n'	
C	d'n	
C	dn'	
D	d'n'	
D	d'n	
D	dn'	
E	d'n'	
E	d'n	
E	dn'	

Step 2: Build a State Table

 


Current State	Input	Next State
A	d'n'	A
A	d'n	B
A	dn'	C
B	d'n'	B
B	d'n	C
B	dn'	D
C	d'n'	C
C	d'n	D
C	dn'	E
D	d'n'	A
D	d'n	B
D	dn'	C
E	d'n'	B
E	d'n	C
E	dn'	D

Step 2: Build a State Table

 

Output	Current State	Input	Next State
c'	A	d'n'	A
	A	d'n	B
	A	dn'	C
c'	B	d'n'	B
	B	d'n	C
	B	dn'	D
c'	C	d'n'	C
	C	d'n	D
	C	dn'	E
c	D	d'n'	A
	D	d'n	B
	D	dn'	C
c	E	d'n'	B
	E	d'n	C
	E	dn'	D

Step 2: Build a State Table

 

**Why do we need
a sequential logic to
build this circuit?**

Output	Current State	Input	Next State
	A	d'n'	A
	A	d'n	B
	A	dn'	C
	B	d'n'	B
	B	d'n	C
	B	dn'	D
	C	d'n'	C
	C	d'n	D
	C	dn'	E
	D	d'n'	A
	D	d'n	B
	D	dn'	C
	E	d'n'	B
	E	d'n	C
	E	dn'	D

Step 2: Build Sequential Circuit

Current State	Input	Next State
A	d'n'	A
A	d'n	B
A	dn'	C
B	d'n'	B
B	d'n	C
B	dn'	D
C	d'n'	C
C	d'n	D
C	dn'	E
D	d'n'	A
D	d'n	B
D	dn'	C
E	d'n'	B
E	d'n	C
E	dn'	D

State Encoding:

5 states: How many bits?

Option 1: 3 bits

Option 2: 1 bit per state ✓

A: 10000
 B: 01000
 C: 00100

One hot encoding

Step 2: Build Sequential Circuit

Current State	Input	Next State
A	d'n'	A
A	d'n	B
A	dn'	C
B	d'n'	B
B	d'n	C
B	dn'	D
C	d'n'	C
C	d'n	D
C	dn'	E
D	d'n'	A
D	d'n	B
D	dn'	C
E	d'n'	B
E	d'n	C
E	dn'	D

One hot encoding

State A = 10000

State B = 01000

State C = 00100


State D = 00010

State E = 00001

D flip-flop

Current State	Next State
0	0
1	1
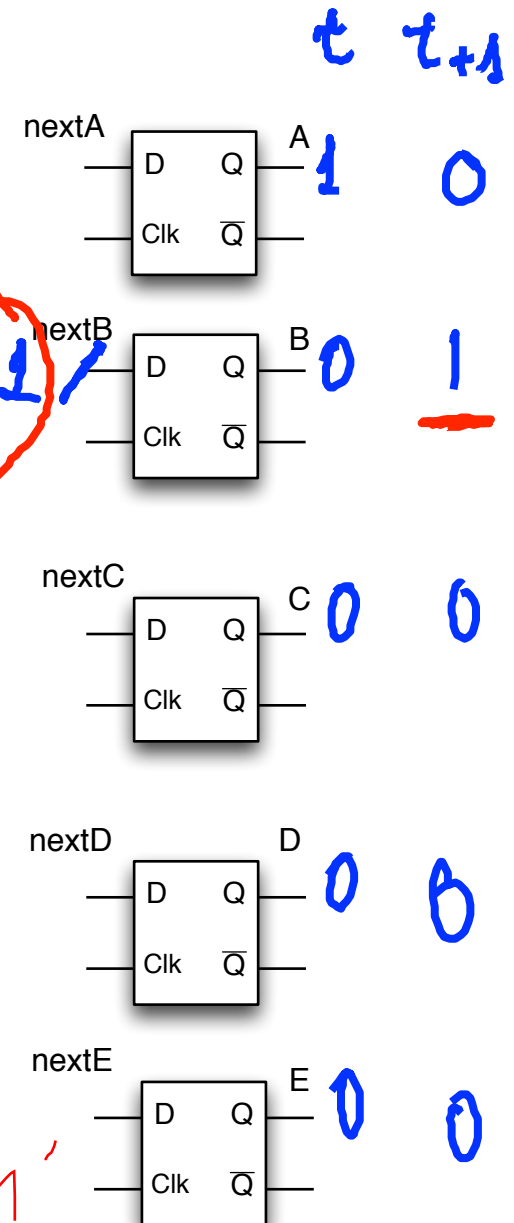
$$\text{nextA} = A \cdot d \cdot n' + D \cdot a \cdot n'$$



Step 2: Build Sequential Circuit

Current State	Input	Next State
A	d'n'	A
A	d'n	B
A	dn'	C
B	d'n'	B
B	d'n	C
B	dn'	D
C	d'n'	C
C	d'n	D
C	dn'	E
D	d'n'	A
D	d'n	B
D	dn'	C
E	d'n'	B
E	d'n	C
E	dn'	D

One hot encoding

State A = 10000

State B = 01000

State C = 00100

State D = 00010

State E = 00001

next D?






A: nextD = $Ad'n' + Dd'n'$

B: nextD = $Ad'n + Bd'n' + Dd'n$

C: nextD = $Bdn' + Cd'n + Edn'$






D: nextD = 1
     
$$\text{nextD} = \bar{E}dn' + \bar{B}dn' + Cdn'$$



Step 2: Build Sequential Circuit

Current State	Input	Next State
A	d'n'	A
A	d'n	B
A	dn'	C
B	d'n'	B
B	d'n	C
B	dn'	D
C	d'n'	C
C	d'n	D
C	dn'	E
D	d'n'	A
D	d'n	B
D	dn'	C
E	d'n'	B
E	d'n	C
E	dn'	D

     

Step 2: Build a State Table

Current State	Input	Next State
A	d'n'	A
A	d'n	B
A	dn'	C
B	d'n'	B
B	d'n	C
B	dn'	D
C	d'n'	C
C	d'n	D
C	dn'	E
D	d'n'	A
D	d'n	B
D	dn'	C
E	d'n'	B
E	d'n	C
E	dn'	D



$$\text{nextA} = Ad'n' + Dd'n'$$

$$\text{nextB} = Ad'n + Bd'n' + Dd'n + Edn'$$


$$\text{nextC} = And' + Bd'n + Cd'n' + Ddn' + Ed'n$$

$$\text{nextD} = Bdn' + Cd'n + Edn'$$

$$\text{nextE} = Cdn'$$

Output: Candy = D + E

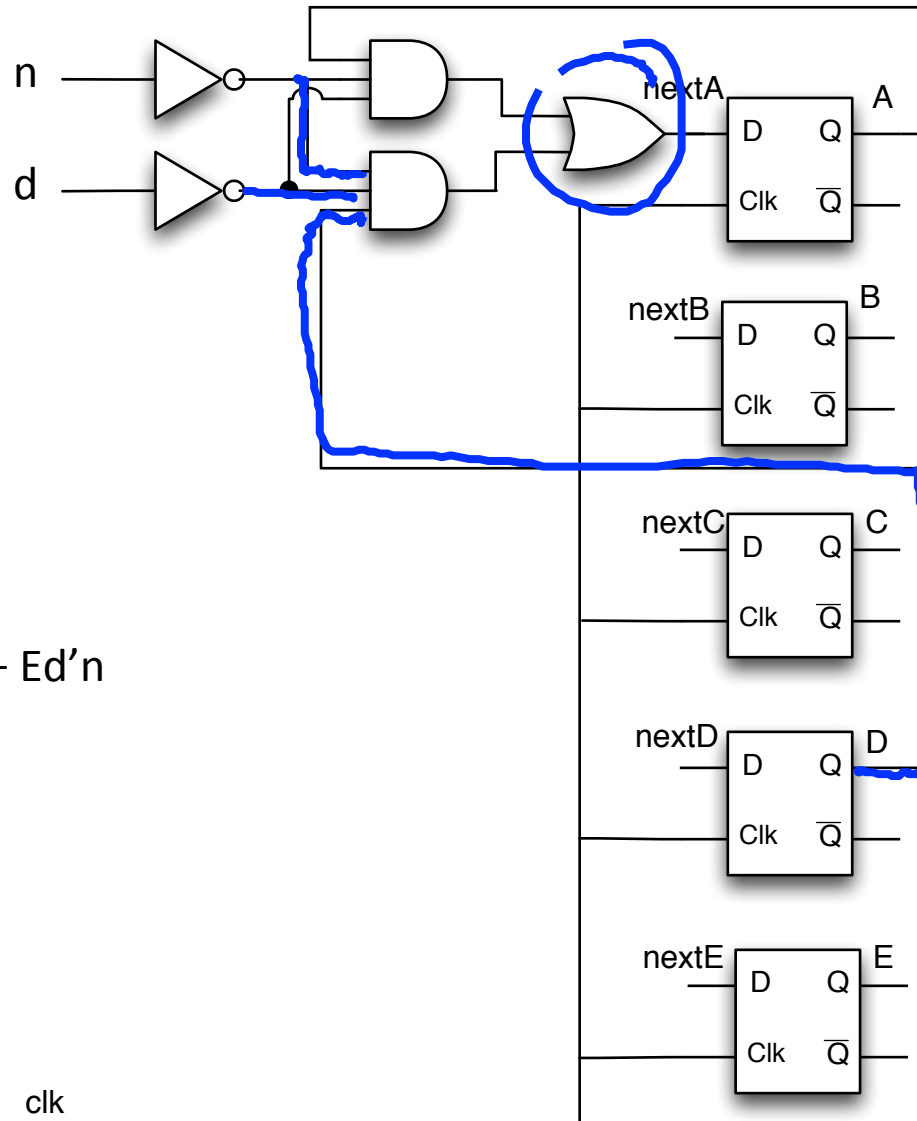
Step 3: Sequential circuit with D flip-flops




$$\begin{aligned} \text{nextA} &= Ad'n' + Dd'n' \\ \text{nextB} &= Ad'n + Bd'n' + Dd'n + Edn' \\ \text{nextC} &= And' + Bd'n + Cd'n' + Ddn' + Ed'n \\ \text{nextD} &= Bdn' + Cd'n + Edn' \\ \text{nextE} &= Cdn' \end{aligned}$$

Output: $c = D + E$

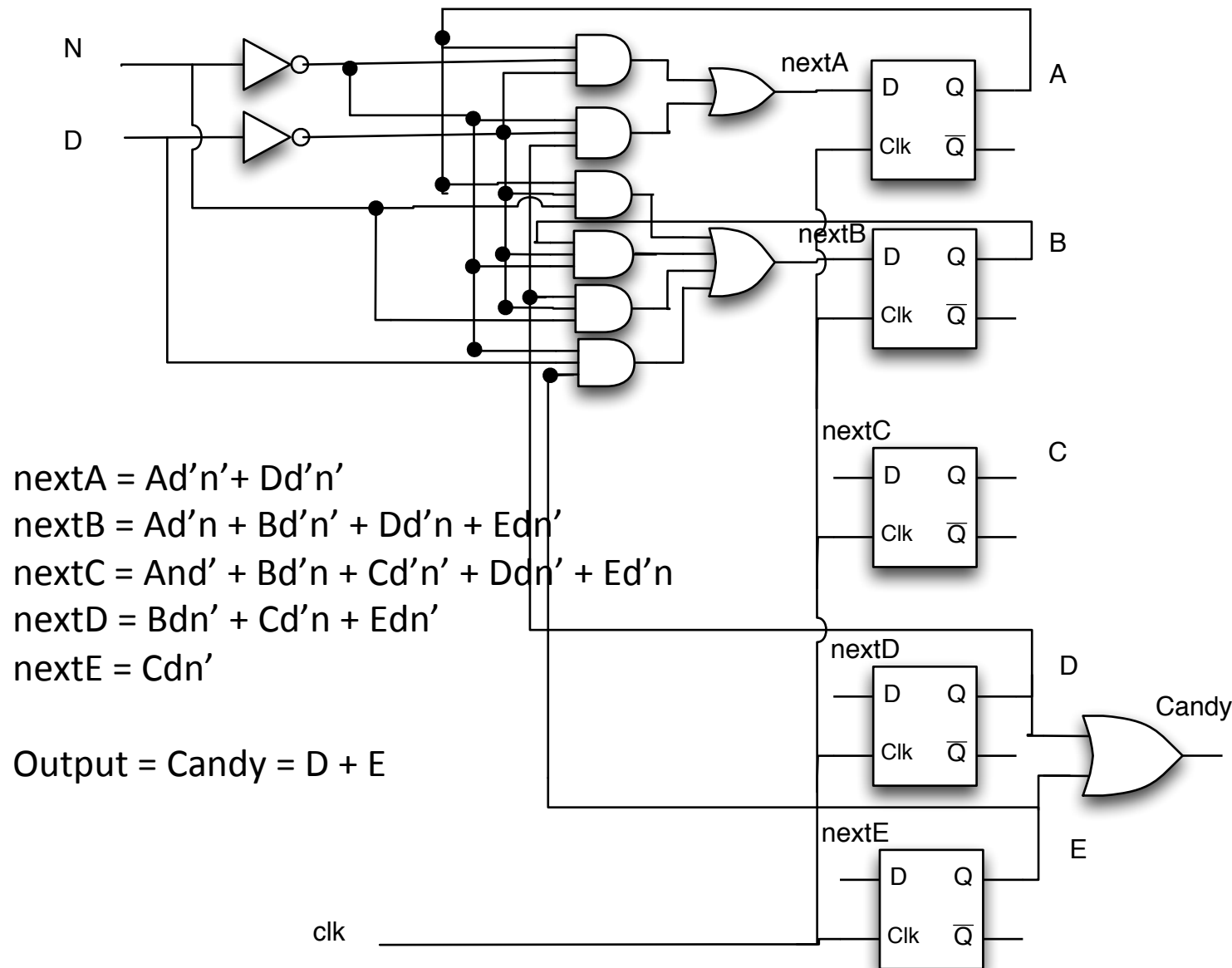
Step 3: Sequential circuit with D flip-flops



Timing Diagram

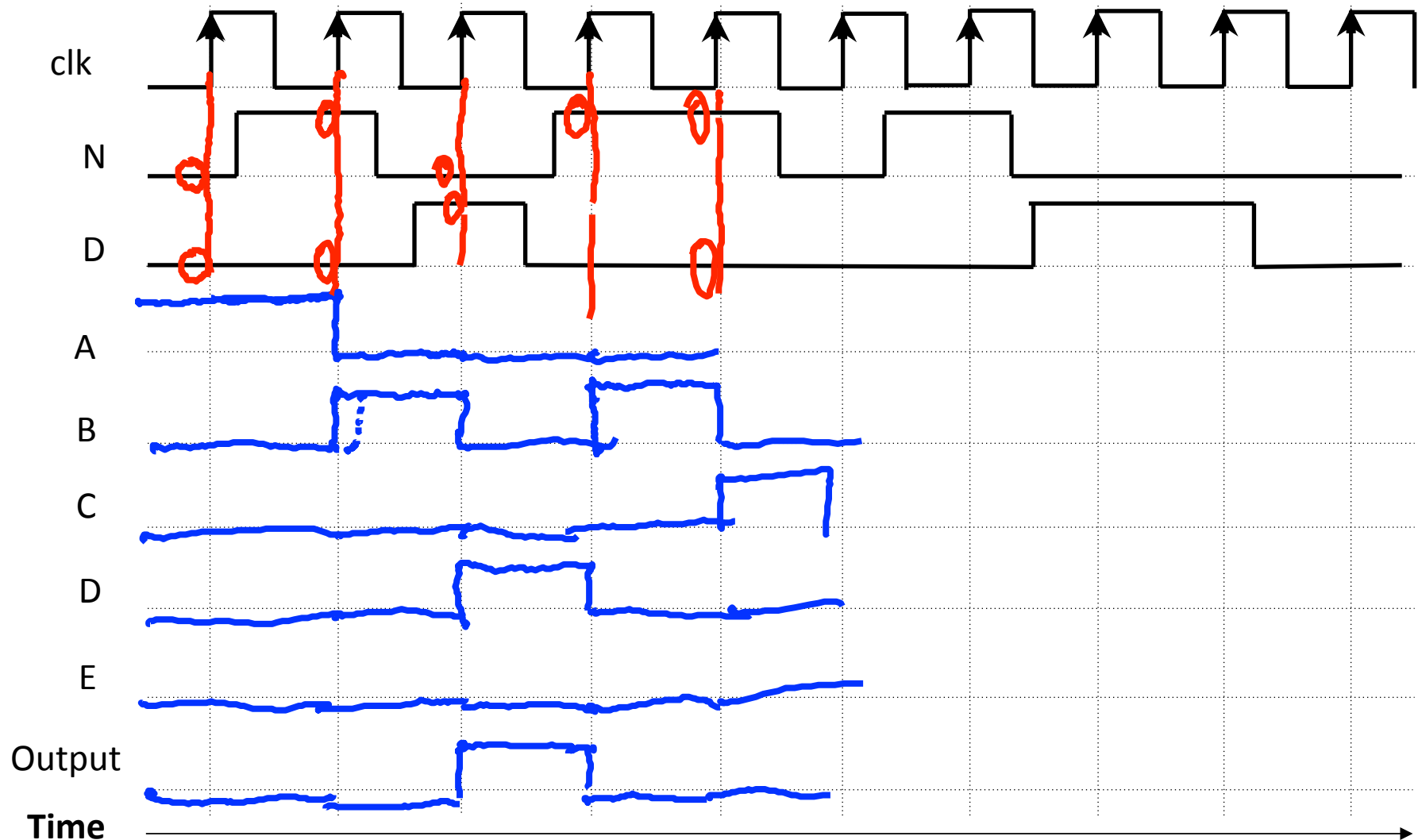

Timing Diagram

 

Another example: Sequence recognizer


- A **sequence recognizer** is a special kind of sequential circuit that looks for a special bit pattern in some input.
- The recognizer circuit has one input, X.
- There is one output, Z, which is 1 when the desired pattern is found.
- Our example will detect the bit pattern “1001”:

Inputs:	1	1	1	0	0	1	1	0	1	0	0	1	0	0	1	1	0	...
Outputs:	0	0	0	0	0	0	1	0	0	0	0	0	1	0	0	1	0	...

Here, one input and one output bit appear every clock cycle.


- This requires a sequential circuit because the circuit has to “remember” the inputs from previous clock cycles, in order to determine whether or not a match was found.

State diagram

 

State	Meaning
A	None of the desired pattern (1001) has been input yet.
B	We've already seen the first bit <u>1</u> of the desired pattern.
C	We've already seen the first two bits <u>10</u> of the desired pattern.
D	We've already seen the first three bits <u>100</u> of the desired pattern.
<u>E</u>	We've seen the pattern <u>1001</u>


State diagram

 

State	Meaning
A	None of the desired pattern (1001) has been input yet.
B	We've already seen the first bit (1) of the desired pattern.
C	We've already seen the first two bits (10) of the desired pattern.
D	We've already seen the first three bits (100) of the desired pattern.
E	We've seen the pattern (1001)

State diagram

 - We need *two* outgoing arrows for each node, to account for the possibilities of $X=0$ and $X=1$.



Inputs: 1 1 1 0 0 1 1 0 1 0 0 1 0 0 1 1 0 ...
 Outputs: 0 0 0 0 0 0 1 0 0 0 0 0 1 0 0 1 0 ...

Transitions for E:

A: $x=0 \rightarrow A$; $x=1 \rightarrow B$


B: $x=0 \rightarrow C$; $x=1 \rightarrow B$

C: $x=0 \rightarrow B$; $x=1 \rightarrow A$

D: $x=0 \rightarrow D$; $x=1 \rightarrow B$


State diagram

 - We need *two* outgoing arrows for each node, to account for the possibilities of $X=0$ and $X=1$.




State diagram

- Need to determine the output

 


State Table

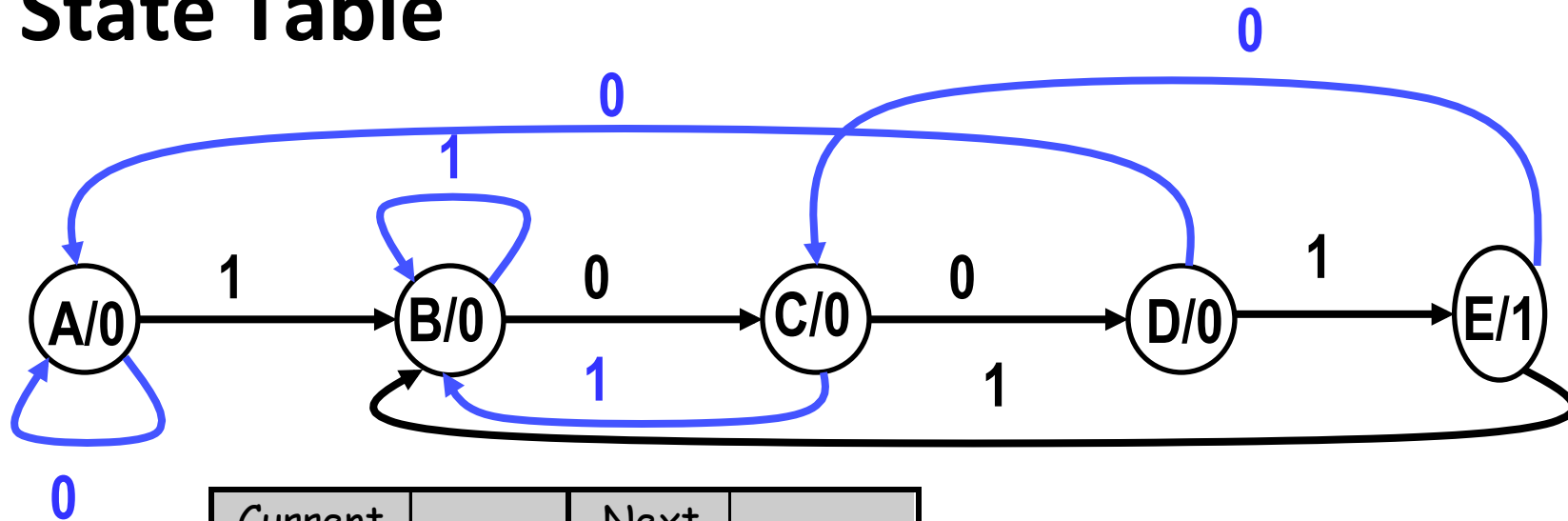

Current State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	E	1
E	0	C	0
E	1	B	0

State Table

 

Current State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	E	1
E	0	C	0
E	1	B	0

$$A_{next} = Ax' + Dx'$$

$$B_{next} = Ax + Bx + Cx + Ex$$

$$C_{next} = Bx' + Ex'$$

$$D_{next} = Cx'$$

$$E_{next} = Dx$$

$$\text{Output} = E$$